

# 《数字电路设计》 期末串讲

Digital Circuit Design

李晨阳

6 月 11 日



## 目录

<b>1</b>	<b>Number System</b>	<b>3</b>
1.1	Conversion . . . . .	3
1.2	Arithmetic . . . . .	4
1.3	Negative Number . . . . .	4
1.3.1	Conversion: Binary $-2'$ s Complement . . . . .	5
1.4	Floating Point Numbers . . . . .	5
1.5	Parity Checking . . . . .	6
<b>2</b>	<b>Logic Function and Switching Algebra</b>	<b>6</b>
2.1	Some Gates . . . . .	6
2.2	Theorems . . . . .	7
<b>3</b>	<b>Karnaugh Maps</b>	<b>8</b>
3.1	Minterm and Maxterm . . . . .	8
3.2	Karnaugh Map . . . . .	9
3.2.1	Prime Implicants . . . . .	11
<b>4</b>	<b>Hazards and Glitches</b>	<b>12</b>
<b>5</b>	<b>Latches and Flip-Flop</b>	<b>13</b>
5.1	SR Latch(NOR gate) . . . . .	13
5.2	$\bar{S} \bar{R}$ Latch . . . . .	14
5.3	D Latch . . . . .	15
5.4	Master-Slave D Flip-Flop . . . . .	15
5.5	Master-Slave JK Flip-Flop . . . . .	16
5.6	Edge-Triggered Flip-Flops . . . . .	16
5.7	Timing parameters . . . . .	17
<b>6</b>	<b>Sequential Circuit Analysis</b>	<b>17</b>
6.1	Structure . . . . .	17
6.2	3 equations and 3 tables . . . . .	18

6.3	Process . . . . .	19
<b>7</b>	<b>Autonomous Sequential Circuit Design</b>	<b>20</b>
7.1	Process . . . . .	21

# 1 Number System

## 1.1 Conversion

- **Hexadecimal (base 16):** Digits in base 16 range from 0 to 15: 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F .
- **MSB:**Most Significant Digit.(rightmost)  
**LSB:**Least Significant Digit.(leftmost)

$$53_{10} = 110101_2$$

- A large binary number to be converted to decimal.(**Binary number-Hex-Decimal**).
- Non-integer conversion: **Integer part:** from LSD to MSD. **Fractional Part:** from MSD to LSD.

### Exercise 1:

Convert 46 to binary.

Convert 265.7810 to hexadecimal.

Convert  $345_{16}$  to binary.

Convert  $111001001010_2$  to Decimal.

## 1.2 Arithmetic

1. Carry to next place when you exceed base!
2. Borrow the base amount when you need to subtract!

EXAMPLE:

```

A 7 3 4 8 6 5
+ 1 2 5 9 D 6
A 8 5 A 2 3 B

```

## 1.3 Negative Number

- **Sign-Magnitude Representation:** Magnitude and symbol representing  $+/ -$ .
- **Two's Complement:**  $n$  bits create a range over  $[-2^{n-1} \dots 2^{n-1} - 1]$ .

Code	Simple	Signed	2's Comp
0000	0	+0	0
0001	1	1	1
0010	2	2	2
0011	3	3	3
0100	4	4	4
0101	5	5	5
0110	6	6	6
0111	7	7	7
1000	8	-0	-8
1001	9	-1	-7
1010	10	-2	-6
1011	11	-3	-5
1100	12	-4	-4
1101	13	-5	-3
1110	14	-6	-2
1111	15	-7	-1

### 1.3.1 Conversion: Binary $-2$ 's Complement

1. Obtain the n-bit simple binary equivalent.
2. Invert the bits of that representation.
3. Add 1 to the result.
4. Copy the sign bit into all the additional bits in the new format if you need to make extension.

#### Exercise 2:

Convert -46 to 8-bit  $2$ 's complement.

Calculate 28-32.(in  $2$ 's Complement).

## 1.4 Floating Point Numbers

### IEEE-754 Format

8-bits		23-bits
<b>s</b>	<b>e</b>	<b>f</b>

**Normal Value** =  $(-1)^s 1.f * 2^{e-127}$

**Denormal Value** =  $(-1)^s 0.f * 2^{1-127}$

#### Exercise 3:

Represent -0.75 in floating point format.

## 1.5 Parity Checking


- Even-parity code: set the parity bit to 0 if there's an even number of 1s; set the parity bit to 1 otherwise.
- Odd-parity code: set the parity bit to 0 if there's an odd number of 1s; set the parity bit to 1 otherwise.

## 2 Logic Function and Switching Algebra

### Switching Algebra:

- Two-valued boolean algebra.
- Basic operations are AND, OR and complement.

### 2.1 Some Gates

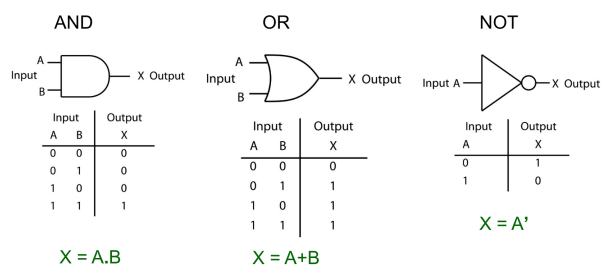

NAND			NOR			XOR			XNOR		
A	B	F	A	B	F	A	B	F	A	B	F
0	0	1	0	0	1	0	0	0	0	0	1
0	1	1	0	1	0	0	1	1	0	1	0
1	0	1	1	0	0	1	0	1	1	0	0
1	1	0	1	1	0	1	1	0	1	1	1
$F = (A \cdot B)'$			$F = (A + B)'$			$F = (A \oplus B)$			$F = (A \oplus B)'$		
						$F = A'B + AB'$			$F = A'B' + AB$		

## 2.2 Theorems

(T1) $X + 0 = X$	(T1') $X \cdot 1 = X$
(T2) $X + 1 = 1$	(T2') $X \cdot 0 = 0$
(T3) $X + X = X$	(T3') $X \cdot X = X$
(T4) $(X')' = X$	
(T5) $X + X' = 1$	(T5') $X \cdot X' = 0$

**De Morgan's Theorems** :Interchanging operations and complement each variable.

$$(T13)(X1 \cdot X2 \cdot \dots \cdot Xn)' = X1' + X2' + \dots + Xn'$$

$$(T13')(X1 + X2 + \dots + Xn)' = X1' \cdot X2' \cdot \dots \cdot Xn'$$

**Principle of Duality**: Only interchange operations.

Example: The dual of  $F = X \cdot Y + Z \cdot W$  is  $F^D = (X + Y) \cdot (Z + W)$ .

**Exercise 4:**

### Two (and Three) Variable Theorems

(T6) $X + Y = Y + X$	(T6') $XY = YX$	(Commutativity)
(T7) $(X + Y) + Z = X + (Y + Z)$	(T7') $(XY)Z = X(YZ)$	(Associativity)
(T8) $XY + XZ = X(Y + Z)$	(T8') $(X + Y)(X + Z) = X + YZ$	(Distributivity)
(T9) $X + XY = X$	(T9') $X(X + Y) = X$	(Covering)
(T10) $XY + XY' = X$	(T10') $(X + Y)(X + Y') = X$	(Combining)
(T11) $XY + X'Z + YZ = XY + X'Z$		(Consensus)

$$(T11') (X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$$

**Absorption Theorem** (not in the textbook):  
 (T\*)  $X + X'Y = X + Y$     (T\*)'  $X(X' + Y) = XY$



All theorems can be proved, either algebraically or through the use of a truth table.



Simplify  $F = [AB'(A + C)]' [(A'B)' + (A + B' + C')]$

Simplify  $F = (A + B)(A + C')(A + D)(BC'D + E)$

### 3 Karnaugh Maps

Another approach to represent (and simplify) Boolean equations.

#### 3.1 Minterm and Maxterm

1. **minterm:**

- A product of n distinctive logic variables (or their complements); e.g.,  $X \cdot Y \cdot Z$ ;
- The sum of minterms corresponds to the combination of Truth Table rows for which the function produces a 1 output;
- Each variable is represented by its complement if the variable value is 0.

2. **maxterm:**

- The sum of n distinctive logic variables or their complements e.g.,  $X+Y+Z$ .

- The product of maxterms corresponds to the product of Truth Table rows for which the function produces a 0 output;
- Each variable is represented by its complement if the variable value is 1.

**EXAMPLE:** Write the boolean function in the form of Sum of Minterms and Product of maxterms.

X	Y	Z	F	$\bar{F}$	
0	0	0	1	0	$m_0$
0	0	1	0	1	$m_1$
0	1	0	1	0	$m_2$
0	1	1	0	1	$m_3$
1	0	0	0	1	$m_4$
1	0	1	1	0	$m_5$
1	1	0	0	1	$m_6$
1	1	1	1	0	$m_7$

### 3.2 Karnaugh Map

**Tips:** The minterm numbers do not follow the normal binary counting order sequence. Only 1 bit changes from one adjacent column to the next.

 


图 1: 2-variable k-map

 


图 2: 3-variable k-map

 


图 3: 4-variable k-map

### Process of simplifying using k-map:

1. Put 1' s in boxes of corresponding terms and put 0' s in all other boxes.
2. group adjacent 1' s (in powers of 2) and eliminate unnecessary variables.
3. Remember to circle the largest groupings possible!

### Exercise 5:

Simplify  $F = X' \cdot Y' \cdot Z' + X' \cdot Y' \cdot Z + X' \cdot Y \cdot Z' + X \cdot Y' \cdot Z' + X \cdot Y' \cdot Z$  using k-map and draw the **NAND** gate implementation.

### 3.2.1 Prime Implicants

When we do grouping, we should always ensure that the size of each group is maximised and the number of groups is minimised to get **minimal sum of products**.

**Prime Implicants:** Largest possible grouping of 1's. (for each 1)

**Essential Prime Implicants:** If any group contains a minterm that isn't also covered by another overlapping group, then that is an EPI.

#### Exercise 6:

Find PIs, EPIs, and the equation.

AB \ CD	00	01	11	10
00	1	0	1	1
01	0	1	1	1
11	0	1	1	1
10	1	0	0	1

**Exercise 7:** Find the minimal sum of products for  $F$  where,  $F = X'Y'Z + X'YZ' + X'YZ + XY'Z' + XY'Z$ .

$\begin{array}{c} \diagup \\ YZ \\ \diagdown \end{array}$	00	01	11	10
X				
0	0	0	0	0
1	0	0	0	0

Don't care:

W X Y Z	F
0 0 0 0	x
0 0 0 1	1
0 0 1 0	x
0 0 1 1	1
0 1 0 0	0
0 1 0 1	x
0 1 1 0	0
0 1 1 1	1
1 0 0 0	0
1 0 0 1	0
1 0 1 0	0
1 0 1 1	1
1 1 0 0	0
1 1 0 1	0
1 1 1 0	0
1 1 1 1	1

$F(W,X,Y,Z) = \Sigma m(1, 3, 7, 11, 15)$   
 $d(W,X,Y,Z) = \Sigma m(0, 2, 5)$

**Answer:**  
 $F = YZ + W'X'$

$\begin{array}{c} \diagup \\ YZ \\ \diagdown \end{array}$	00	01	11	10
WX				
00	x	1	1	x
01	0	x	1	0
11	0	0	1	0
10	0	0	1	0

## 4 Hazards and Glitches

**Output glitch:** A momentary unexpected output change (short pulse) when an input changes; usually caused by gate propagation delays.

**Hazards:** A timing hazard exists in a combinational circuit when it produces an output glitch when one or more inputs change.


### Find adjacent groups!

- A **static-1 hazard** is a pair of input combinations that: (i) differ in only one input variable and (ii) both give a 1 output; such that it is possible for a momentary 0 output to occur during a transition in the differing input variable.
- A **static-0 hazard** is a pair of input combinations that: (i) differ in only one input variable and (ii) both give a 0 output; such that it is possible for a momentary 1 output to occur during a transition in the differing input variable.

**Exercise 8:** Is there any static hazard on  $F = A'D' + A'B'C' + ABC + ACD$ ?

## 5 Latches and Flip-Flop

### 5.1 SR Latch(NOR gate)

 


Inputs		Outputs	
S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

Undefined operation when both inputs are **True**.


Oscillation occurs if both S and R return to 0 simultaneously!



### SR Latch with Control Input (2/2)

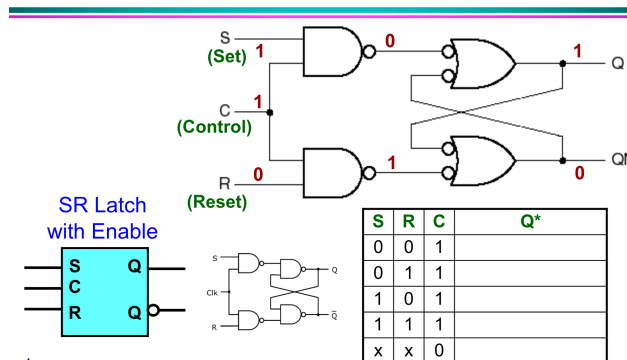


## 5.2 $\bar{S} \bar{R}$ Latch

 

 
**Exercises 9:** Draw the outputs of an SR latch for the input waveforms shown below.

Assume that the propagation delay of a NOR gate is 10ns.



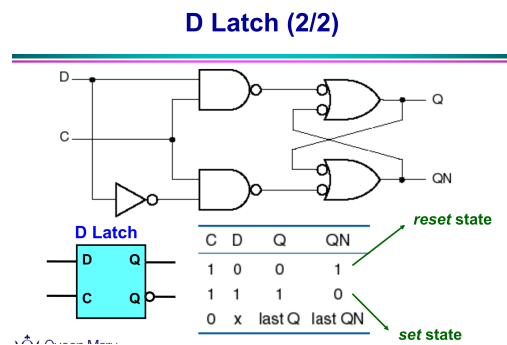
### 5.3 D Latch

- Can eliminate the indeterminate state by ensuring that both Set and Reset inputs are never equal to '1' at the same time!
- Has only two inputs: Data (D) and Control (C).




### 5.4 Master-Slave D Flip-Flop

 



## 5.5 Master-Slave JK Flip-Flop


No indeterminate state!

 

J	K	C	Q	QN
x	x	0		
0	0	1		
0	1	1		
1	0	1		
1	1	1		




 - 1's Catching: Output changes to 1 even though K and not J is asserted at the end of the triggering pulse.
- 0's Catching: Output changes to 0 even though J and not K is asserted at the end of the triggering pulse.



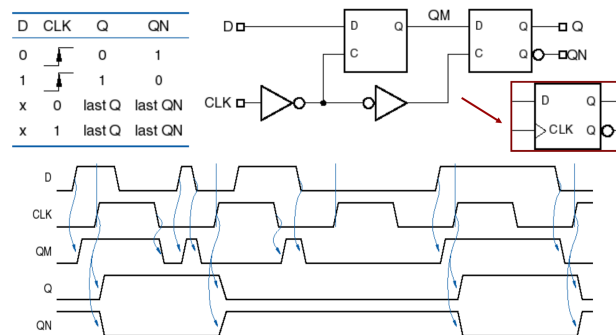
## 5.6 Edge-Triggered Flip-Flops

Ignore inputs while the clock pulse is at a constant level. Only set outputs on clock pulse transitions. Thus solving the catching problems.



 
## 5.7 Timing parameters

- Propagation Delay
- recovery time(SR Latch)
- setup time
- hold time



## 6 Sequential Circuit Analysis

### 6.1 Structure

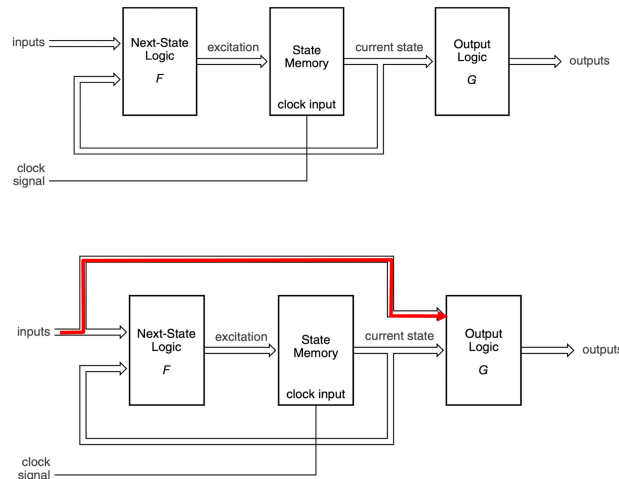

## 6.2 3 equations and 3 tables

- **Input Equation(excitation).** A boolean equation expressed by Next-state logic , in terms of the input to the state memory. equation
- **Characteristic Equation.** Determined by the characteristic equation for the flip-flop type.


<b>Device Type</b>	<b>Characteristic Equation</b>
S-R Latch MS S-R Flip-Flop	$Q^* = S + R'Q$
D Latch	$Q^* = D$
JK Latch MS J-K Flip-Flop ET J-K Flip-Flop	$Q^* = JQ' + K'Q$
ET D Flip-Flop	$Q^* = D$
D Flip-Flop w/ Enable	$Q^* = E_N D + E_N' Q$
T Flip-Flop	$Q^* = Q'$
T Flip-Flop w/ Enable	$Q^* = E_N Q' + E_N' Q$

- **Output Equation**
- **Transition Table:** Expresses the next state as a function of the current state and the input.
- **State Table:** Expresses the next state as a function of the current state and the input using alphanumeric state names.
- **State/Output Table:** Similar to the State Table, but includes the output as well.


### 6.3 Process

1. Obtain the *input* (or *excitation*) **equations**.
2. Obtain the **output equations**.
3. Obtain the *next state* (or *characteristic*) **equations**.
4. Substitute the *input equations* into the *next state equations* to obtain **transition equations**.
5. Develop a **transition table** from the *transition equations*.
6. Develop a **state table** that relates the possible states in terms of the *present* and *next state*.
7. Develop a **state/output table** that relates the possible states in terms of the *present* and *next state*, together with the *outputs*.
8. Draw the **state diagram**.

**Exercise 10:** Analyze the following sequential circuit, draw the transition diagram.

 

 **Exerciese 11:** Analyze the following sequential circuit, draw the transition diagram.



## 7 Autonomous Sequential Circuit Design

Autonomous circuits do not have primary inputs, they have only secondaries (plus a clock signal).

## 7.1 Process

1. Draw-up a table of present and next states. Need to take account of the characteristic equation of the flip-flop
2. Draw a Karnaugh map for each next state output (flip-flop input) in terms of the present state.
3. Minimise the logic using Karnaugh map simplification
4. Draw-up the corresponding circuit diagram for the FSM.

**Exercise 12:** Design a 6-state counter using the first six binary numbers. Use JK flip-flops.

**Exercise 13:** Design a ring adder with an effective cycle state of 100-010-001-100.

**谢谢!**

**祝大家取得好成绩!**